
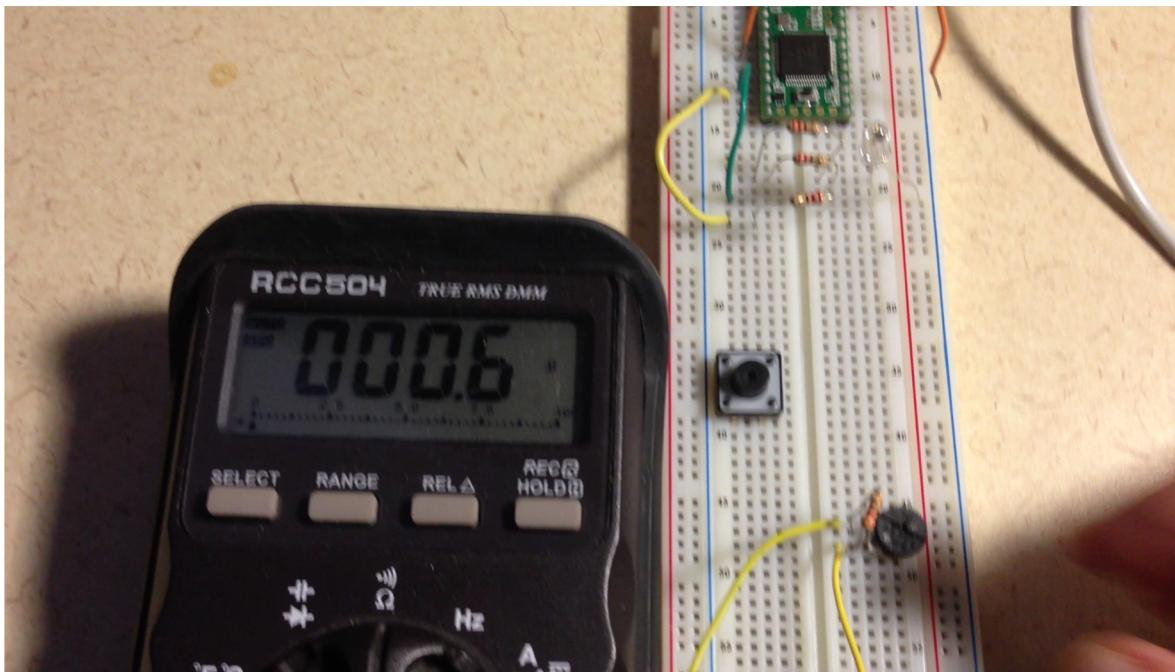


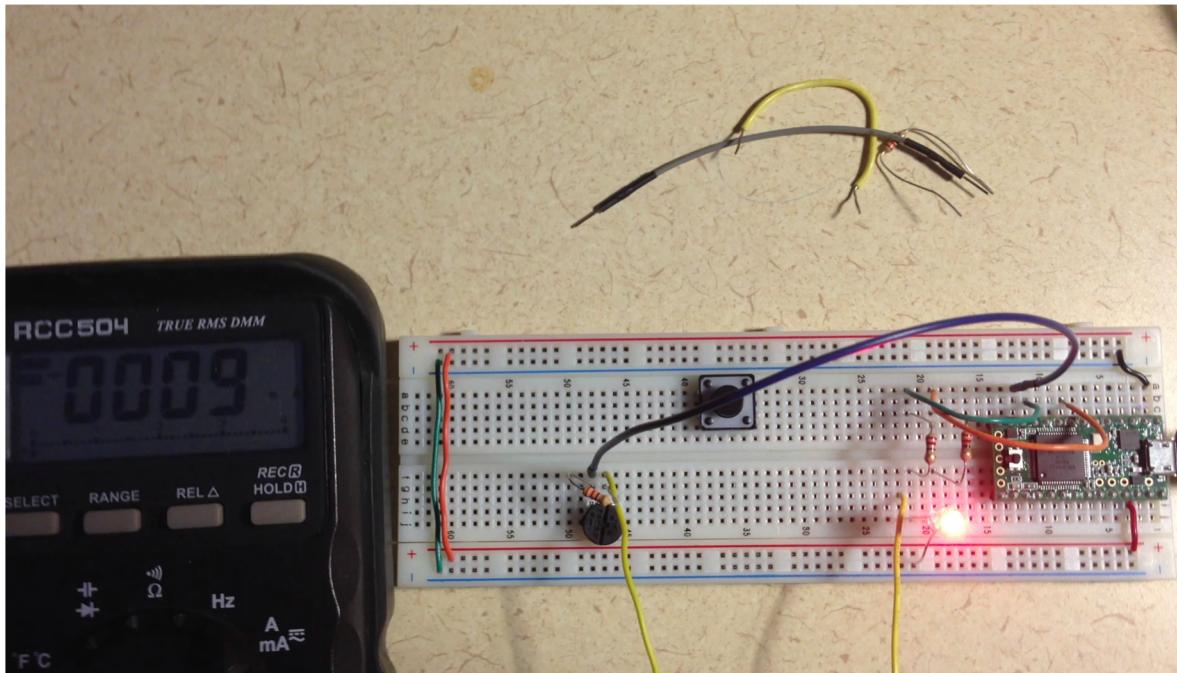
Use the $10k\Omega$ pot in parallel with the 220Ω resistor




Install parallel resistance into path of red LED



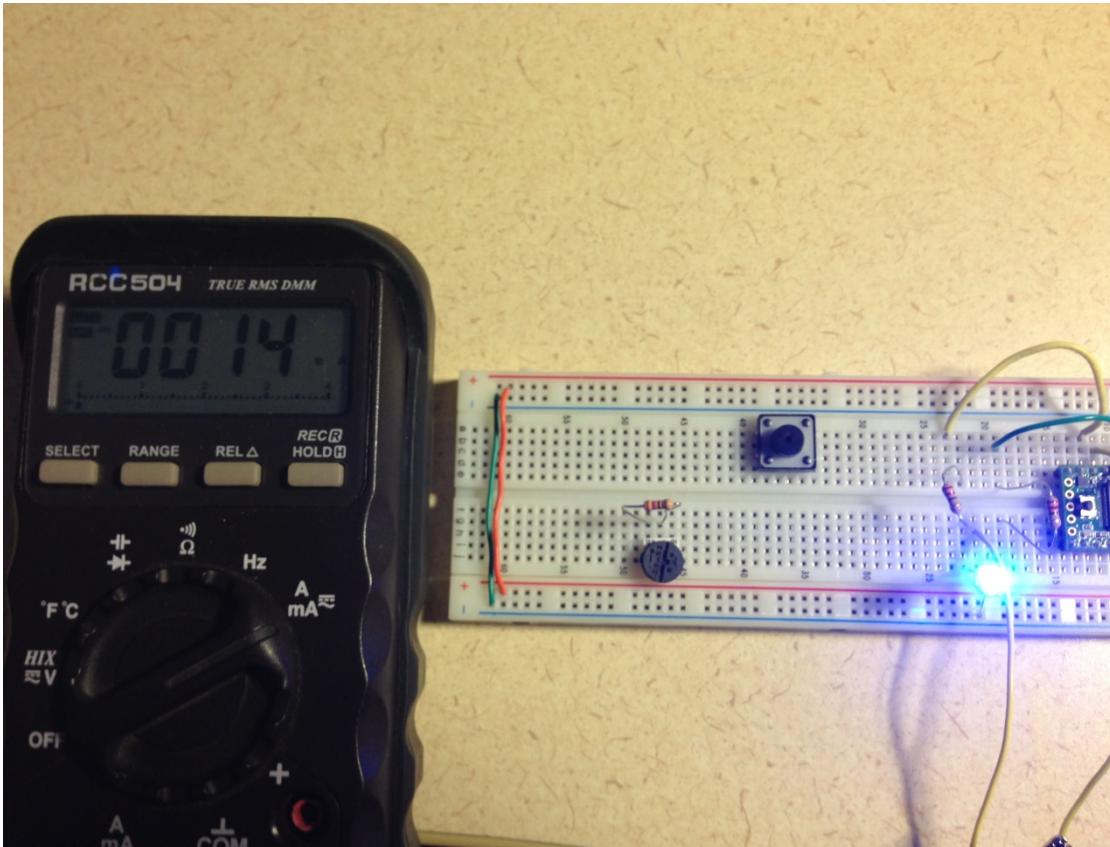Blue LED draws about 14 mA with no Resistor in Series



Green LED + Current Draw

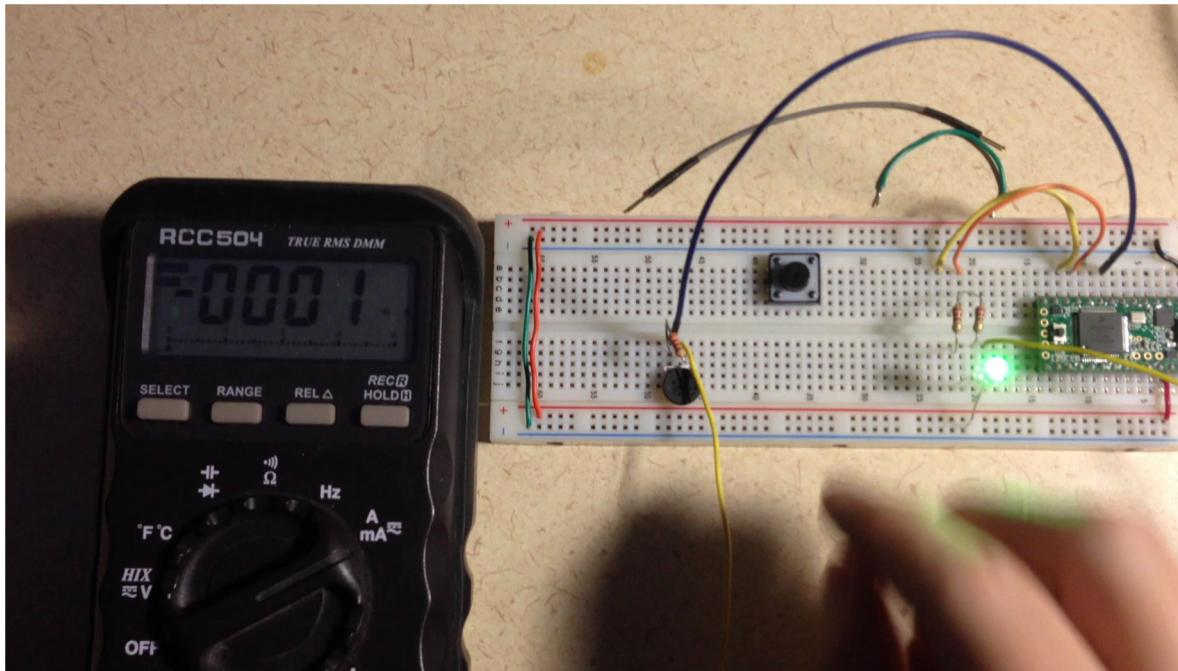

Blue LED + Current Draw

